



**LUND**  
UNIVERSITY

Electrical and Information Technology

# Integrated A/D and D/A Converters (ETIN55)

## Lab2 Manual

Martin Anderson  
Pietro Andreani

February/October 2021

## Lab 2 – Analog Modeling with Verilog-A

This lab will introduce the procedure of modelling and simulating analog circuits using the hardware describing language **Verilog-A**. Your behavioral code will be simulated using the analog circuit simulator *spectre*, which is the same simulator that is used for simulating analog circuits in Cadence.

### Laboratory report

Include all plotted simulation results, the schematics and answers to all questions in your laboratory report.

### Homework exercises

1. Go through the slides from the lab seminar.
2. Read carefully the tasks to be performed in this lab.
3. Download the VerilogA manual from </usr/local-eit/cad2/cadence/ic616/doc/verilogamsref/verilogamsref.pdf>, and read the sections relevant to this lab.
4. A parallel RLC resonator circuit has  $R = 10\text{ k}\Omega$ ,  $C = 10\text{ pF}$  and  $L = 100\text{ nH}$ . At what frequency will the impedance be peaking?
5. Write down the truth table of a NAND gate.

## Laboratory exercises

### Part 1: Model and simulate an RLC resonance circuit

A parallel resonance circuit consists of a resistor, a capacitor and an inductor in parallel. In this part, you shall model the behavior (impedance) of this circuit using Verilog-A.

 


Figure 1. RLC resonator test bench.

#### 1. Preliminary steps:

- a. Log into a UNIX workstation.
- b. Create a Cadence directory in your home directory, for example CDSLAB, and descend into it:  

```
> mkdir CDSLAB  
> cd CDSLAB
```
- c. Download the zip file VerilogALab.zip from the course homepage, and unzip it in your Cadence directory:  

```
> unzip VerilogALab.zip
```
- d. If you are working on a UNIX workstation in the undergraduate lab or in the research lab: while in your Cadence directory, start **Cadence**:  

```
> initdde adda21  
> virtuoso &
```
- e. If a window appears asking “**Would you like to try checking out the Licence Virtuoso\_Schematic\_Editor\_XL**” (or something analogous), click on **Yes** (repeatedly, if necessary).
- f. Select *Tools > Library Manager...* in the **Virtuoso** window to open the *Library Manager* window if it did not start automatically. Add the **VerilogALab** library to your library path in the *Library Manager* with *Edit > Library Path...* Save your changes to the library path when done.

#### 2. Create a **Verilog-A** model of an **RLC circuit**:

- a. Create the **RLC instance** in the **VerilogALab** library by selecting *File > New > Cell view...* in the **Library Manager**. Name your circuit **RLC** and select **verilogA** in the **View** field by choosing **verilogA** in the scroll-down window for **Type**. Then click **OK**.
- b. In the **emacs** window that pops up, enter the **verilogA** code for the RLC resonance circuit:  

```
// VerilogA for VerilogALabSol, RLC, verilogA
```

```

#include "constants.vams"
#include "disciplines.vams"
module RLC(a,b);
  inout a,b;
  electrical a,b;
  parameter real R = 10k;
  parameter real L = 0.1u;
  parameter real C = 10p;
  // Model the behavior here !!!
endmodule

```

- c. To compile the code, save it and close the **emacs** window. If there are errors, you will be asked if you want to correct them. Answer *yes*.
- d. After editing and correcting all the errors, save the file and quit. A message “*Cellview RLC symbol does not exist*” will appear. Choose *yes* to generate the symbol view of instance **RLC**. Specify the pins *a* and *b* in the new window (Figure 2) and generate the symbol. Click **OK**.

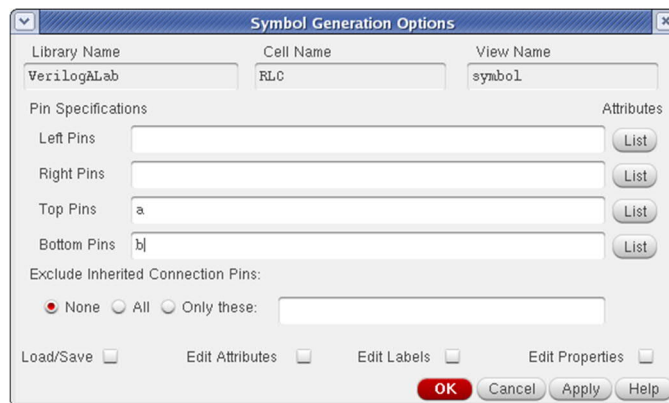


Figure 2. The **Symbol Generation Options** window.

- e. In the **Symbol Editor** view, you can modify the symbol as you like. For example, you can reuse already existing symbols by choosing *Create > Import Symbol...* and selecting the symbol of the cell you want to use. For the **RLC** circuit, combine the symbol views of the **res**, **cap** and **ind** cells of the **analogLib** library. Remove all pins, *cds parameters* etc (i.e., everything except the drawings in green) from the imported symbols. Be sure to use your own pins, *a* and *b*. Save your symbol and quit.
3. Simulate the **RLC** circuit and verify the operation of your model. Since it is a *Verilog-A* module, *spectre* can be used to simulate it:
    - a. To simulate the **verilogA** description of the **RLC** circuit, a test bench shall be used. Create a new cell view **RLC\_Tb** and create a **schematic** view of it. Instantiate a current source **isin** and a ground **gnd** from the library **analogLib**. Instantiate your **RLC** circuit from your own design library. Set the **AC Magnitude** of the current source to 1 (A). The resulting test bench is shown in Figure 1.
    - b. In the **Schematic** window, select *Launch > ADE L*. If a **Next License** window appears, click on **Yes** (repeatedly, if necessary). In the **Virtuoso Analog Design Environment**

- (ADE) window, make sure that **veriloga** is in the **Switch View List** by clicking *Setup > Environment...* and adding **veriloga** in the **Switch View List**, if needed.
- Click on *Analysis > Choose...* and select an **ac** analysis from 1Hz to 300MHz according to the following: the *Sweep Variable* is **Frequency** (default); the *Sweep Range* is 1 (**Start**) to 300M (**Stop**); choose *Sweep Type > Linear* and set the **Number of Steps** to 1000 (double-check that you did not select **Step Size** instead of **Number of Steps**).
  - In **ADE**, select *Outputs > To be plotted > Select on Schematic*. Select the **A** net (and not the **a** node!) in the **schematic**. Does your **ADE** look like the one below?

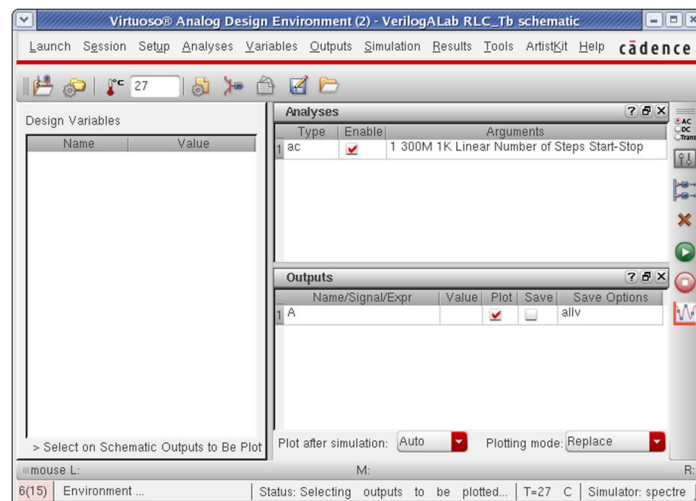


Figure 3. The ADE (Analog Design Environment) window for AC simulation of the RLC circuit.

- Click *Simulation > Netlist and Run* (green button on the right margin of the ADE window) to run the simulation. The results should look like in Figure 4.

 


Figure 4. Simulation result for the RLC circuit.

- Add a  $10\Omega$  parasitic resistance in series with the capacitor and  $5\Omega$  in series with the inductor by changing your **veriloga** code, introducing two extra nodes and writing KCL equations for them as well. Rerun the simulation. Include the simulation results in your report.

## Part 2: Modeling a digital NAND gate

Digital functionality can also be modeled using **Verilog-A**. In this lab module, you will model a digital **NAND** gate with the possibility of specifying delay time, rise time, and fall time.

The NAND gate shall have the two inputs **A** and **B** and the output **Y**. Use two integer variables, **logica** and **logicb**, to save the state of the **A** and **B** inputs. When **V(A)** or **V(B)** cross the threshold on a rising edge, **logica** or **logicb** = 1. When **V(A)** or **V(B)** cross the threshold on a falling edge, **logica** or **logicb** = 0.

Recall that the function **@(cross(V(A) - thresh, +1))** detects when the voltage on **A** crosses the threshold **thresh** on a rising edge. If the event is reached, the action is executed.

Use the **transition** statement to describe the output **Y**, which has delay time **td**, rise time **tr**, and fall time **tf**. The defaults shall be **td=2n**, **tr=1n**, **tf=1n**.

### 4. Create the **veriloga** view of cell **NAND1**:

- Click *File > New > Cellview* in the Cadence **Virtuoso** window. Select **NAND1** as the cell name and **veriloga** as view name. Cancel the **Invoke Modelwriter** form if it appears.
- Write the code for the NAND gate. Let the code below guide you.

```
// VerilogA for VerilogALab, NAND1, veriloga
#include "constants.vams"
#include "disciplines.vams"

module NAND1(A,B,Y);
  inout A,B;
  output Y;
  electrical A,B,Y;

  parameter real vlogic_high = 1.0;
  parameter real vlogic_low = 0.0;
  parameter real td = 2n, tr=1n, tf=1n;

  Write the veriloga code modeling the NAND here!

endmodule
```

- Save the changes and close the text editor. If there are no errors, a window appears and asks you if you want to create the associated symbol. Click **Yes**.
- Modify the **NAND1** symbol if you are not satisfied by the default. Save the symbol and exit the symbol editor.

### 5. Create a test bench for your design:

- Create the cell **NAND1\_Tb**, view **schematic**.
- A blank schematic window appears. Instantiate your **NAND1** cell, an output pin, and two **vpwlf** voltage generators and a **gnd** from **analogLib**. Add the wire names **Ain** and **Bin**. The schematic should look like the one in Figure 5.
- To set the properties of the **NAND1**: click on the instance and press **q** on the keyboard and select **veriloga** for **CDF Parameter of view** close to the bottom of the window (the default may be **Use Tools Filter**). Set **td=4ns**, **tr=5ns**, **tf=10ns**.
- For the **V0** voltage generator, write **Apwl** in the field **Pwl file name**. For **V1**, write **Bpwl** in the same field. The files **Apwl** and **Bpwl** are found in the **stim/** directory (which was contained in **VerilogALab.zip**).

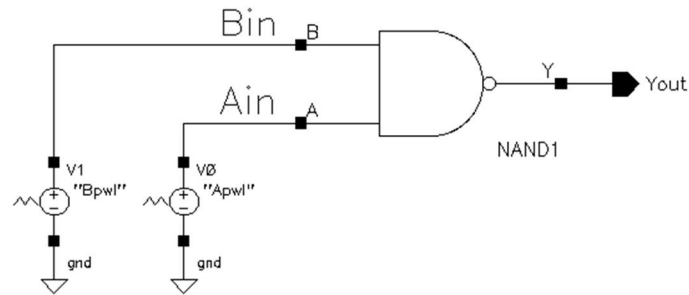


Figure 5. Test bench schematic for **NAND1**.

6. Simulate your test bench:

- Start the **ADE** from your test bench schematic.
- Set up a **tran** (transient) analysis with **Stop Time** of **6us**, with **moderate** accuracy.
- Set up a relative path to the stimulus files by selecting *Setup > Simulation Files ...* in the **ADE** and adding **./stim** to the **Include Path** field.
- Set up the outputs to be plotted with *Outputs > To Be Plotted > Select On Schematic*. Select the **Ain**, **Bin** and **Yout** nets. Press **ESC** while cursor is still inside the schematic.
- Select *Simulation > Netlist* and *Run* to start the simulation.
- When the simulation finishes, the transient signals at **Ain**, **Bin** and **Yout** are plotted. Verify that the operation of **NAND1** is correct, including delays and rise/fall times. Repeat the simulation with **td=40ns** and **tr=tf=100ns**, and check that the plots change as expected. Save the result for your lab report.

 


Figure 6. Simulation results for **NAND1** (use *Graph > Split Current Strip* in the **Visualization** window to plot the three waveforms as above – by default, they share the same y-axis)

### Part 3: Creating a frequency measuring device

In the following, you will create a circuit module that measures the frequency of a single-tone input signal. You will plot the results and write the value of the measured frequency to a file. Furthermore, you will use this module to measure the frequency of a VCO.

Your module shall have three terminals: **vp**, **vn** and **fout**. The frequency of the signal between **vp** and **vn** will be measured and sent to **fout**. Make this measurement by detecting the times at which the last two zero crossings occurred. You may want to use some real variables inside your **veriloga** description.

For a frequency meter, you could just output a voltage proportional to the frequency by measuring the period of the input signal and inverting the value. However, to show how **natures** and **disciplines** work, in this lab you will use a new **nature** *Frequency*, and a new **discipline** *freq\_current*. **Verilog-A** uses access functions to output information. Normally, those are **V** for voltage and **I** for current. *Frequency* has to have its own access function, which is called **FF** in the definitions below. These definitions could be added to the *disciplines.vams* file, but in this lab they will be added within the module itself.

```
nature Frequency
    abstol = 1m;
    access = FF;
    units = "Hz";
endnature

discipline freq_current
    potential Frequency;
    flow Current;
enddiscipline
```

In addition, your module will use an integer flag, **log\_to\_file**, to determine when to write the output data to a file. When **log\_to\_file=0**, no data log file is written. When **log\_to\_file=1**, the output time and frequency data are written to the file “**%C:r.dat**”, which is

*~/simulation/FreqMeter\_Tb/spectre/schematic/netlist/input.dat*

Insert a header at the top of your file, such as “**#Time/Freq data from module ‘%M’**”. Insert also a closing line at the end of it, and close it at the end of your circuit module.

More specifically, do the following:

#### 7. Define the **FreqMeter veriloga** module:

- Create a **veriloga** view for a cell named **FreqMeter**.
- Use and modify the veriloga code below by filling in the comments in **boldface** with suitable code.

```
// VerilogA for VerilogALab, FreqMeter, veriloga
#include "constants.vams"
#include "disciplines.vams"

nature Frequency
    abstol = 1m;
    access = FF;
    units = "Hz";
endnature
```



```

discipline freq_current
    potential Frequency;
    flow Current;
enddiscipline

module FreqMeter(vp, vn, fout);
    electrical vp,vn;
    freq_current fout;
    parameter integer log_to_file = 0;
    // define local variables here !!!
analog begin
    @(initial_step) begin
        if (log_to_file) begin
            // create the open file statements here !!!
        end
    end
    @(cross(V(vp,vn), +1)) begin
        // setup the crossing statements here !!!
        if (log_to_file) begin
            // log the output to your file here !!!
            // use the function $fstrobe(file,"formats",variables)
            // E.g., format %-.10g for each variable gives a
            // precision of 10 digits
        end
    end
    // contribute the output to fout here !!!
end
endmodule

```

- c. Save your code and exit the text editor. Iterate until the **Verilog-A** syntax check is ok.
  - d. When all errors are fixed, create the symbol with **vp** and **vn** to the left and **fout** to the right. Save the symbol and close the symbol editor.
8. Create a test bench for the frequency meter:
- a. Create a new cell called **FreqMeter\_Tb** with view name schematic.
  - b. Instantiate the **FreqMeter** cell you just created and the **SweptSine** component from the current **VerilogALab** library; build your schematic as in Figure 7.

 


Figure 7. Test bench schematic for **FreqMeter**.

- c. Set **log\_to\_file=1** for the **FreqMeter** (click on the instance, press **q** and select **veriloga** for **CDF Parameter of view**).
  - d. Set **StartFreq=1k** and **HertzPerSecond= 10k** for the **SweptSine** instance.
  - e. *Check and Save* the schematic.
9. Simulate the frequency meter:
- a. Start the **ADE**, and set up a transient analysis of **100ms**.
  - b. Set up the outputs to be plotted by clicking *Outputs > To Be Plotted > Select On Schematic* and select the **sine\_in** and **Freq** signals.
  - c. Select *Simulation > Netlist* and *Run* to run the simulation.
  - d. In the **Visualization** window, check that the frequency at **100ms** is approximately **2 kHz**, as expected. Check that all data has been written correctly in *~/simulation/FreqMeter\_Tb/spectre/schematic/netlist/input.dat*. The file should contain two columns, with simulation time and calculated frequency, respectively.
  - e. Save your results for your lab report.

#### Part 4: Create a VCO Verilog-A model

Open the **VCO** (voltage-controlled oscillator) cell and understand the algorithm described by the verilog code.

10. Build a test bench to test the VCO:

- Create a new cell **VCO\_Tb** with a **schematic** view.
- Instantiate the **VCO** and the **FreqMeter** from your lab library as well as one **vpwl** voltage generator and a **gnd** symbol from the **analogLib** library. The schematic should look like in Figure 8.

 


Figure 8. Test bench schematic for VCO.

- Set the properties of the **vpwl** source: **Number of pairs of points** is 2, **Time 1** is 0, **Voltage 1** is -1.0, **Time 2** is 1, and **Voltage 2** is 1.0.
- Set the properties of the VCO instance: **vco\_amp=1.0**, **vco\_cf=1.5k**, **vco\_gain=1.0k** and **vco\_ppc=40**.
- Set the properties of the **FreqMeter**: **log\_to\_file=0**.

11. Simulate the VCO:

- Start the **ADE** and set up a transient analysis with **Stop Time = 1s**, with **Accuracy** set to **conservative**.
- Click **Outputs > To Be Plotted > Select on Schematic**. Select the **VcoVin**, **VcoOut** and **Freq** nets. Use the **ESC** key to end the selection process.
- Select **Simulation > Netlist** and **Run** to start the simulation.
- In the waveform window, check the frequency as you did in the previous lab. It should measure **500Hz** at **-1.0V** and **2500Hz** at **+1.0V** and look like in Figure 9 (to visualize three distinct waveforms, use the command **Graph > Split Current Strip** in the **Visualization** window).

 


Figure 9. Simulation results for VCO.

## Part 5: Create and simulate a look-up table model of a diode

In this part, you will extract a look-up table and write a verilog look-up table based model of a diode. The table model will then be compared to the diode from the **cmos065** library.

### 12. Create the diode test bench:

- a. Create a new cell view called **Diode\_Tb** with a schematic view. Instantiate a **vdc** from **analogLib** and a **dnlvgtgp** N+/Pwell diode from the library **cmos065**. Set both **Length** and **Width** of the diode to **1um**. It should look like in Figure 10.

 


Figure 10. Test bench schematic for the **dnlvgtgp** diode table extraction.

- b. Set the **DC Voltage** of the voltage source to a variable **Vdiode** that you can sweep in the simulation.
- ### 13. Simulate test bench to extract the table model:
- a. Start the **ADE** and import the design variables by clicking on *Variables > Copy from Cellview*. Set **Vdiode** to **0mV**.
  - b. Setup a **dc analysis**. Click on **Design Variable** and type **Vdiode** in the **Variable Name** field. Sweep **Vdiode** from **0V** to **1V**; choose **Sweep Type** as **Linear** and set **Number of Steps** to **100**.
  - c. Choose *Outputs > To Be Plotted > Select from Schematic* and select the net **Vd**, as well as the current entering the diode by clicking on the diode anode terminal.
  - d. In the **ADE**, select *ArtistKit > Setup Corners...*; in the window that appears, find the **Select All** field, where there are three scroll-down menus. Under **GLOBAL VARIATIONS**, choose **<all typical>**; under **LOCAL VARIATIONS**, choose **no**; under **LIBRARY**, choose **DK**. Click now on the **Save Model File** button close to the top of the window, after which you close the window.
  - e. Run the dc analysis with *Simulation > Netlist* and *Run*.
  - f. Open the calculator by clicking *Tools > Calculator ...* in the **ADE**.
  - g. Referring to Figure 11: Select the **wave** field and thereafter click on the diode current waveform in the **Visualization** window to import it into the Calculator; click on the field indicated in Figure 11 (red arrow on the right) to create a look-up table with the values of the diode current vs. the input voltage. The result of this operation is shown in Figure 12.
  - h. Save the look-up table to a file with *File > Export* choosing **SPECTRE** as file type.

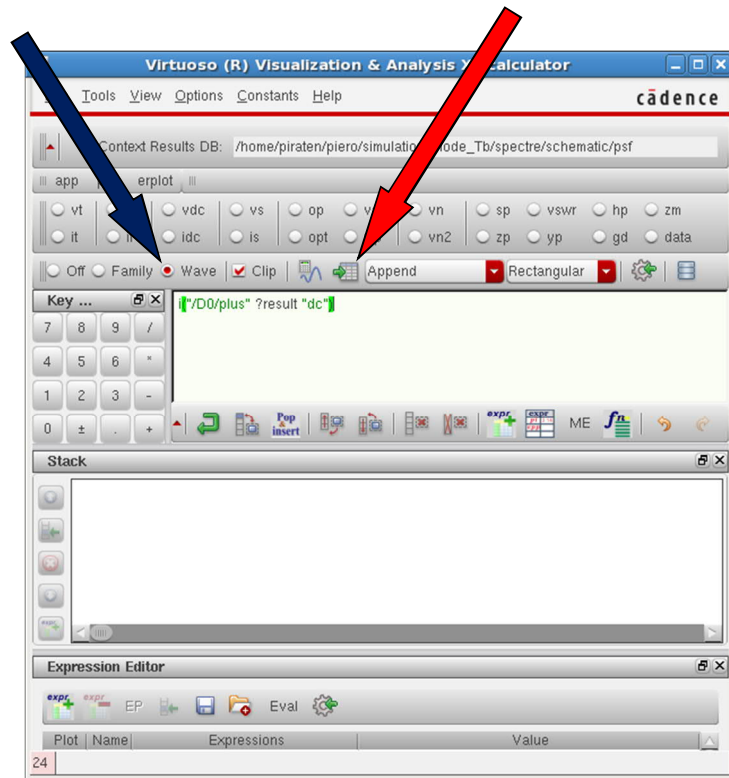


Figure 11. The **Calculator** window.

	Vdiode	i("/D0/...c") (A)
1	0.000	0.000
2	10.00E-3	10.18E-15
3	20.00E-3	20.30E-15
4	30.00E-3	30.39E-15
5	40.00E-3	40.44E-15
6	50.00E-3	50.48E-15
7	60.00E-3	60.51E-15
8	70.00E-3	70.52E-15
9	80.00E-3	80.53E-15
10	90.00E-3	90.54E-15
11	100.0E-3	100.5E-15
12	110.0E-3	110.6E-15
13	120.0E-3	120.6E-15
14	130.0E-3	130.6E-15
15	140.0E-3	140.6E-15
16	150.0E-3	150.6E-15
17	160.0E-3	160.6E-15
18	170.0E-3	170.6E-15

Figure 12. The **Table** window.

14. Write the **veriloga** diode model:

- Create a new cell called **MyDiode** with a **veriloga** view.
- Edit your **veriloga** code starting from the following module:  

```
// VerilogA for VerilogALabSol, MyDiode, veriloga
```

```

'include "constants.vams"
'include "disciplines.vams"

module MyDiode(p,n);
  inout p,n;
  electrical p,n;

  analog begin
    // Model Id(Vd) here !!!
  end
endmodule.

```

- c. Create a symbol by importing the **dnltgtp** symbol from **cmos065** and edit it.

15. Update the test bench:

- a. Open **Diode\_Tb** and instantiate your **MyDiode** module into the test bench in parallel with **dnltgtp**. The test bench should now look like in Figure 13.

 


Figure 13. Test bench schematic for MyDiode.

16. Simulate the look-up table model:

- Change the dc **Sweep Range** to **Automatic** (instead of **100 points**). The simulator will now interpolate between the values in the table. However, since the number of points in the table is relatively large, you will not see a large difference.
- Select the anode current of **MyDiode** to be plotted as well.
- Click on *Simulation > Netlist and Run* to run the simulation.
- Check that the **dnltgtp** and **MyDiode** currents are the same. They should look something like the plots in Figure 14 (the two curves are basically coincident).
- Extend the dc sweep to **1.05V**, and use different ways of interpolating the current curve for the values beyond the look-up table limits (possible interpolation methods are **clamp**, **linear**, and three different **spline curves**). Compare the results.

 


Figure 14. Simulation result for **dnlvtgp** and **MyDiode**.